

Unit-II

Combinational Circuits

Combinational circuit is a circuit in which we combine the different gates in the circuit, for example encoder, decoder, multiplexer and demultiplexer. Some of the characteristics of combinational circuits are following –

- The output of combinational circuit at any instant of time, depends only on the levels present at input terminals.
- The combinational circuit do not use any memory. The previous state of input does not have any effect on the present state of the circuit.
- A combinational circuit can have an n number of inputs and m number of outputs.

Block diagram




We're going to elaborate few important combinational circuits as follows.

Half Adder

Half adder is a combinational logic circuit with two inputs and two outputs. The half adder circuit is designed to add two single bit binary number A and B. It is the basic building block for addition of two **single** bit numbers. This circuit has two outputs **carry** and **sum**.


Block diagram

 

Truth Table

| Inputs | | Output | |
|--------|---|--------|---|
| A | B | S | C |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |


Circuit Diagram

 

Full Adder

Full adder is developed to overcome the drawback of Half Adder circuit. It can add two one-bit numbers A and B, and carry c. The full adder is a three input and two output combinational circuit.


Block diagram

 

Truth Table

| Inputs | | | Output | |
|--------|---|-----------------|--------|----|
| A | B | C _{in} | S | Co |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

Circuit Diagram

 


N-Bit Parallel Adder

The Full Adder is capable of adding only two single digit binary number along with a carry input. But in practical we need to add binary numbers which are much longer than just one bit. To add two n-bit binary numbers we need to use the n-bit parallel adder. It uses a number of full adders in cascade. The carry output of the previous full adder is connected to carry input of the next full adder.

4 Bit Parallel Adder

In the block diagram, A₀ and B₀ represent the LSB of the four bit words A and B. Hence Full Adder-0 is the lowest stage. Hence its C_{in} has been permanently made 0. The rest of the connections are exactly same as those of n-bit parallel adder is shown in fig. The four bit parallel adder is a very common logic circuit.

Block diagram

 


N-Bit Parallel Subtractor

The subtraction can be carried out by taking the 1's or 2's complement of the number to be subtracted. For example we can perform the subtraction $(A-B)$ by adding either 1's or 2's complement of B to A . That means we can use a binary adder to perform the binary subtraction.

4 Bit Parallel Subtractor

The number to be subtracted (B) is first passed through inverters to obtain its 1's complement. The 4-bit adder then adds A and 2's complement of B to produce the subtraction. $S_3 S_2 S_1 S_0$ represents the result of binary subtraction $(A-B)$ and carry output C_{out} represents the polarity of the result. If $A > B$ then $C_{out} = 0$ and the result of binary form $(A-B)$ then $C_{out} = 1$ and the result is in the 2's complement form.

Block diagram

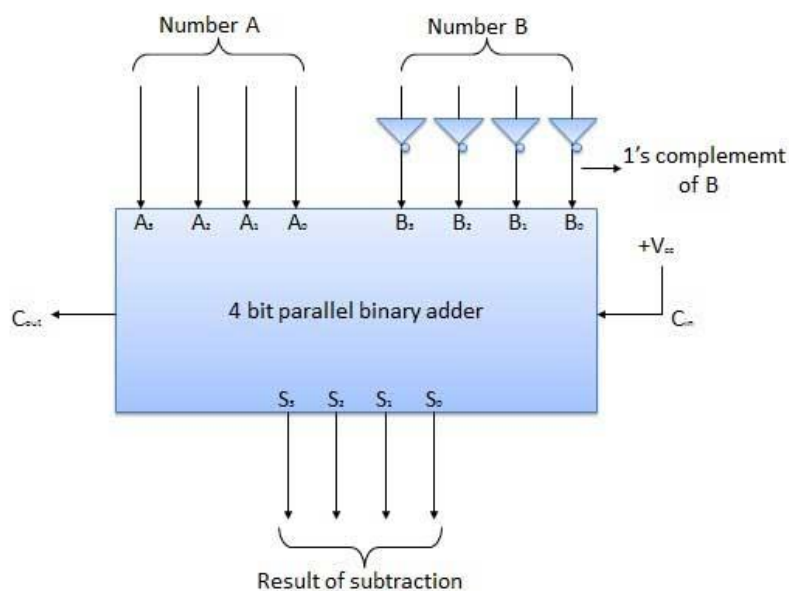


Half Subtractors

Half subtractor is a combination circuit with two inputs and two outputs (difference and borrow). It produces the difference between the two binary bits at the input and also produces an output (Borrow) to indicate if a 1 has been borrowed. In the subtraction (A-B), A is called as Minuend bit and B is called as Subtrahend bit.

Truth Table

| Inputs | | Output | |
|--------|---|---------|--------|
| A | B | (A - B) | Borrow |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

Circuit Diagram

 


Full Subtractors

The disadvantage of a half subtractor is overcome by full subtractor. The full subtractor is a combinational circuit with three inputs A,B,C and two output D and C'. A is the 'minuend', B is 'subtrahend', C is the 'borrow' produced by the previous stage, D is the difference output and C' is the borrow output.

Truth Table

| Inputs | | | Output | |
|--------|---|---|---------|----|
| A | B | C | (A-B-C) | C' |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |


Circuit Diagram

 

Multiplexers

Multiplexer is a special type of combinational circuit. There are n -data inputs, one output and m select inputs with $2^m = n$. It is a digital circuit which selects one of the n data inputs and routes it to the output. The selection of one of the n inputs is done by the selected inputs. Depending on the digital code applied at the selected inputs, one out of n data sources is selected and transmitted to the single output Y . E is called the strobe or enable input which is useful for the cascading. It is generally an active low terminal that means it will perform the required operation when it is low.


Block diagram

 

Multiplexers come in multiple variations

- 2 : 1 multiplexer
- 4 : 1 multiplexer
- 16 : 1 multiplexer
- 32 : 1 multiplexer

Block Diagram

 

Truth Table

| Enable | Select | Output |
|--------|--------|----------------|
| E | S | Y |
| 0 | x | 0 |
| 1 | 0 | D ₀ |
| 1 | 1 | D ₁ |

x = Don't care


Demultiplexers

A demultiplexer performs the reverse operation of a multiplexer i.e. it receives one input and distributes it over several outputs. It has only one input, n outputs, m select input. At a time only one output line is selected by the select lines and the input is transmitted to the selected output line. A de-multiplexer is equivalent to a single pole multiple way switch as shown in fig.

Demultiplexers comes in multiple variations.

- 1 : 2 demultiplexer
- 1 : 4 demultiplexer
- 1 : 16 demultiplexer
- 1 : 32 demultiplexer

Block diagram

 

Truth Table


| Enable | Select | Output |
|--------|--------|-------------------------------|
| E | S | Y ₀ Y ₁ |
| 0 | x | 0 0 |
| 1 | 0 | 0 D _{in} |
| 1 | 1 | D _{in} 0 |

x = Don't care

Decoder

A decoder is a combinational circuit. It has n input and to a maximum $m = 2^n$ outputs. Decoder is identical to a demultiplexer without any data input. It performs operations which are exactly opposite to those of an encoder.

Block diagram

 


Examples of Decoders are following.

- Code converters
- BCD to seven segment decoders
- Nixie tube decoders
- Relay actuator

2 to 4 Line Decoder

The block diagram of 2 to 4 line decoder is shown in the fig. A and B are the two inputs where D through D are the four outputs. Truth table explains the operations of a decoder. It shows that each output is 1 for only a specific combination of inputs.


Block diagram

 

Truth Table

| Inputs | | Output | | | |
|--------|---|----------------|----------------|----------------|----------------|
| A | B | D ₀ | D ₁ | D ₂ | D ₃ |
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |


Logic Circuit

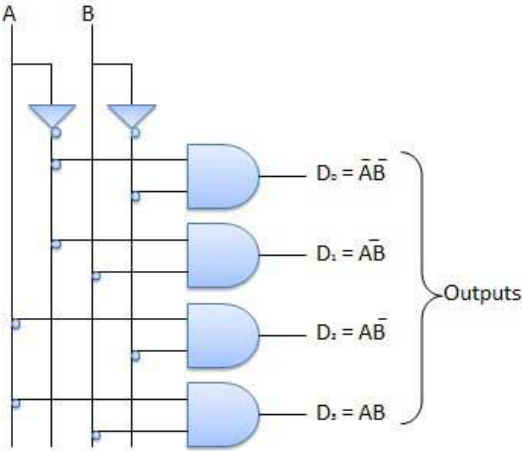

Encoder

Encoder is a combinational circuit which is designed to perform the inverse operation of the decoder. An encoder has n number of input lines and m number of output lines. An encoder produces an m bit binary code corresponding to the digital input number. The encoder accepts an n input digital word and converts it into an m bit another digital word.

Block diagram

 


Examples of Encoders are following.

- Priority encoders
- Decimal to BCD encoder
- Octal to binary encoder
- Hexadecimal to binary encoder

Priority Encoder

This is a special type of encoder. Priority is given to the input lines. If two or more input line are 1 at the same time, then the input line with highest priority will be considered. There are four input D_0, D_1, D_2, D_3 and two output Y_0, Y_1 . Out of the four input D_3 has the highest priority and D_0 has the lowest priority. That means if $D_3 = 1$ then $Y_1 Y_2 = 11$ irrespective of the other inputs. Similarly if $D_3 = 0$ and $D_2 = 1$ then $Y_1 Y_0 = 10$ irrespective of the other inputs.


Block diagram

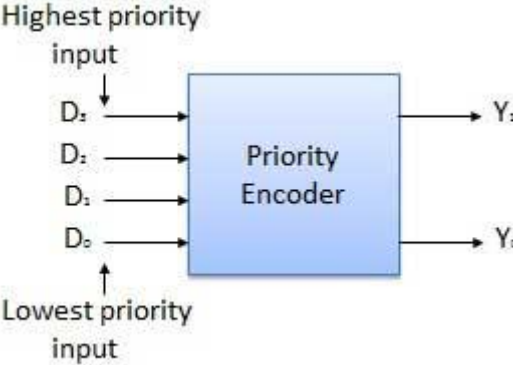

Truth Table

| Highest | Inputs | | Lowest | Outputs | |
|---------|--------|-------|--------|---------|-------|
| D_2 | D_2 | D_1 | D_2 | Y_2 | Y_1 |
| 0 | 0 | 0 | 0 | x | x |
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | x | 0 | 1 |
| 0 | 1 | x | x | 1 | 0 |
| 1 | x | x | x | 1 | 1 |

Logic Circuit

 

Sequential Circuit


Flip Flop

Flip flop is a sequential circuit which generally samples its inputs and changes its outputs only at particular instants of time and not continuously. Flip flop is said to be edge sensitive or edge triggered rather than being level triggered like latches.


S-R Flip Flop

It is basically S-R latch using NAND gates with an additional **enable** input. It is also called as level triggered SR-FF. For this, circuit in output will take place if and only if the enable input (E) is made active. In short this circuit will operate as an S-R latch if $E = 1$ but there is no change in the output if $E = 0$.

Block Diagram

 

Circuit Diagram

 

Truth Table

| Inputs | | | Outputs | | Comments |
|--------|---|---|-----------|----------------------|---------------|
| E | S | R | Q_{n+1} | \overline{Q}_{n+1} | |
| 1 | 0 | 0 | Q_n | \overline{Q}_n | No change |
| 1 | 0 | 1 | 0 | 1 | Rset |
| 1 | 1 | 0 | 1 | 0 | Set |
| 1 | 1 | 1 | x | x | Indeterminate |

Operation


| S.N. | Condition | Operation |
|------|------------------------------|--|
| 1 | S = R = 0 : No change | <p>If $S = R = 0$ then output of NAND gates 3 and 4 are forced to become 1.</p> <p>Hence R' and S' both will be equal to 1. Since S' and R' are the input of the basic S-R latch using NAND gates, there will be no change in the state of outputs.</p> |

| | | |
|---|----------------------------|---|
| 2 | S = 0, R = 1, E = 1 | <p>Since $S = 0$, output of NAND-3 i.e. $R' = 1$ and $E = 1$ the output of NAND-4 i.e. $S' = 0$.</p> <p>Hence $Q_{n+1} = 0$ and $Q_{n+1} \text{ bar} = 1$. This is reset condition.</p> |
| 3 | S = 1, R = 0, E = 1 | <p>Output of NAND-3 i.e. $R' = 0$ and output of NAND-4 i.e. $S' = 1$.</p> <p>Hence output of S-R NAND latch is $Q_{n+1} = 1$ and $Q_{n+1} \text{ bar} = 0$. This is the set condition.</p> |
| 4 | S = 1, R = 1, E = 1 | <p>As $S = 1, R = 1$ and $E = 1$, the output of NAND gates 3 and 4 both are 0 i.e. $S' = R' = 0$.</p> <p>Hence the Race condition will occur in the basic NAND latch.</p> |

Master Slave JK Flip Flop

Master slave JK FF is a cascade of two S-R FF with feedback from the output of second to input of first. Master is a positive level triggered. But due to the presence of the inverter in the clock line, the slave will respond to the negative level. Hence when the clock = 1 (positive level) the master is active and the slave is inactive. Whereas when clock = 0 (low level) the slave is active and master is inactive.

Circuit Diagram

 

Truth Table

| Inputs | | | Outputs | | Comments |
|--------|---|---|------------------|----------------------|-----------|
| E | J | K | Q_{n+1} | \overline{Q}_{n+1} | |
| 1 | 0 | 0 | Q_n | \overline{Q}_n | No change |
| 1 | 0 | 1 | 0 | 1 | Rset |
| 1 | 1 | 0 | 1 | 0 | Set |
| 1 | 1 | 1 | \overline{Q}_n | Q_n | Toggle |

Operation

| S.N. | Condition | Operation |
|------|------------------------------------|---|
| 1 | J = K = 0 (No change) | When clock = 0, the slave becomes active and master is inactive. But since the S and R inputs have not changed, the slave outputs will also remain unchanged. Therefore outputs will not change if J = K = 0. |
| 2 | J = 0 and K = 1 (Reset) | <p>Clock = 1 – Master active, slave inactive. Therefore outputs of the master become $Q_1 = 0$ and $Q_1 \text{ bar} = 1$. That means S = 0 and R = 1.</p> <p>Clock = 0 – Slave active, master inactive. Therefore outputs of the slave become $Q = 0$ and $Q \text{ bar} = 1$.</p> <p>Again clock = 1 – Master active, slave inactive. Therefore even with the changed outputs $Q = 0$ and $Q \text{ bar} = 1$ fed back to master, its output will be $Q_1 = 0$ and $Q_1 \text{ bar} = 1$. That means S = 0 and R = 1.</p> <p>Hence with clock = 0 and slave becoming active the outputs of slave will remain $Q = 0$ and $Q \text{ bar} = 1$. Thus we get a stable output from the Master slave.</p> |
| 3 | J = 1 and K = 0 (Set) | <p>Clock = 1 – Master active, slave inactive. Therefore outputs of the master become $Q_1 = 1$ and $Q_1 \text{ bar} = 0$. That means S = 1 and R = 0.</p> <p>Clock = 0 – Slave active, master inactive. Therefore outputs of the slave become $Q = 1$ and $Q \text{ bar} = 0$.</p> <p>Again clock = 1 – then it can be shown that the outputs of the slave are stabilized to $Q = 1$ and $Q \text{ bar} = 0$.</p> |
| 4 | J = K = 1 (Toggle) | Clock = 1 – Master active, slave inactive. Outputs of master will toggle. So S and R also will be inverted. |

| | | |
|--|--|--|
| | | <p>Clock = 0 – Slave active, master inactive. Outputs of slave will toggle.</p> <p>These changed output are returned back to the master inputs. But since clock = 0, the master is still inactive. So it does not respond to these changed outputs. This avoids the multiple toggling which leads to the race around condition. The master slave flip flop will avoid the race around condition.</p> |
|--|--|--|


Delay Flip Flop / D Flip Flop

Delay Flip Flop or D Flip Flop is the simple gated S-R latch with a NAND inverter connected between S and R inputs. It has only one input. The input data is appearing at the output after some time. Due to this data delay between i/p and o/p, it is called delay flip flop. S and R will be the complements of each other due to NAND inverter. Hence $S = R = 0$ or $S = R = 1$, these input condition will never appear. This problem is avoid by $SR = 00$ and $SR = 1$ conditions.

Block Diagram



Circuit Diagram

 

Truth Table

| Inputs | | Outputs | | Comments |
|--------|---|-----------|----------------------|----------|
| E | D | Q_{n+1} | \overline{Q}_{n+1} | |
| 1 | 0 | 0 | 1 | Rset |
| 1 | 1 | 1 | 0 | Set |


Operation

| S.N. | Condition | Operation |
|------|------------------------|--|
| 1 | E = 0 | Latch is disabled. Hence no change in output. |
| 2 | E = 1 and D = 0 | If E = 1 and D = 0 then S = 0 and R = 1. Hence irrespective of the present state, the next state is $Q_{n+1} = 0$ and $Q_{n+1} \text{ bar} = 1$. This is the reset condition. |
| 3 | E = 1 and D = 1 | If E = 1 and D = 1, then S = 1 and R = 0. This will set the latch and $Q_{n+1} = 1$ and $Q_{n+1} \text{ bar} = 0$ irrespective of the present state. |


Toggle Flip Flop / T Flip Flop

Toggle flip flop is basically a JK flip flop with J and K terminals permanently connected together. It has only input denoted by **T** as shown in the Symbol Diagram. The symbol for positive edge triggered T flip flop is shown in the Block Diagram.

Symbol Diagram

 

Block Diagram

 

Truth Table

| Inputs | | Outputs | | Comments |
|--------|---|------------------|----------------------|-----------|
| E | T | Q_{n-1} | \overline{Q}_{n-1} | |
| 1 | 0 | Q_n | \overline{Q}_n | No change |
| 1 | 1 | \overline{Q}_n | Q_n | Toggle |

Operation

| S.N. | Condition | Operation |
|------|--------------------|---|
| 1 | $T = 0, J = K = 0$ | The output Q and Q bar won't change |
| 2 | $T = 1, J = K = 1$ | Output will toggle corresponding to every leading edge of clock signal. |

Digital Registers

Flip-flop is a 1 bit memory cell which can be used for storing the digital data. To increase the storage capacity in terms of number of bits, we have to use a group of flip-flop. Such a group of flip-flop is known as a **Register**. The **n-bit register** will consist of **n** number of flip-flop and it is capable of storing an **n-bit** word.


The binary data in a register can be moved within the register from one flip-flop to another. The registers that allow such data transfers are called as **shift registers**. There are four mode of operations of a shift register.

- Serial Input Serial Output
- Serial Input Parallel Output
- Parallel Input Serial Output
- Parallel Input Parallel Output

Serial Input Serial Output


Let all the flip-flop be initially in the reset condition i.e. $Q_3 = Q_2 = Q_1 = Q_0 = 0$. If an entry of a four bit binary number 1 1 1 1 is made into the register, this number should be applied to **D_{in}** bit with the LSB bit applied first. The D input of FF-3 i.e. D_3 is connected to serial data input **D_{in}**. Output of FF-3 i.e. Q_3 is connected to the input of the next flip-flop i.e. D_2 and so on.

Block Diagram

 


Operation

 
Before application of clock signal, let $Q_3 Q_2 Q_1 Q_0 = 0000$ and apply LSB bit of the number to be entered to D_{in} . So $D_{in} = D_3 = 1$. Apply the clock. On the first falling edge of clock, the FF-3 is set, and stored word in the register is $Q_3 Q_2 Q_1 Q_0 = 1000$.



 
Apply the next bit to D_{in} . So $D_{in} = 1$. As soon as the next negative edge of the clock hits, FF-2 will set and the stored word change to $Q_3 Q_2 Q_1 Q_0 = 1100$.



 Apply the next bit to be stored i.e. 1 to D_{in} . Apply the clock pulse. As soon as the third negative clock edge hits, FF-1 will be set and output will be modified to $Q_3 Q_2 Q_1 Q_0 = 1110$.



 Similarly with $D_{in} = 1$ and with the fourth negative clock edge arriving, the stored word in the register is $Q_3 Q_2 Q_1 Q_0 = 1111$.




Truth Table

| | CLK | $D_n = Q_3$ | $Q_3 = D_2$ | $Q_2 = D_1$ | $Q_1 = D_0$ | Q_0 |
|-----------|-----|-------------|-------------|-------------|-------------|-------|
| Initially | | | 0 | 0 | 0 | 0 |
| (i) | ↓ | 1 | 1 | 0 | 0 | 0 |
| (ii) | ↓ | 1 | 1 | 1 | 0 | 0 |
| (iii) | ↓ | 1 | 1 | 1 | 1 | 0 |
| (iv) | ↓ | 1 | 1 | 1 | 1 | 1 |

→ Direction of data travel


Waveforms

 

Serial Input Parallel Output

- In such types of operations, the data is entered serially and taken out in parallel fashion.
- Data is loaded bit by bit. The outputs are disabled as long as the data is loading.
- As soon as the data loading gets completed, all the flip-flops contain their required data, the outputs are enabled so that all the loaded data is made available over all the output lines at the same time.
- 4 clock cycles are required to load a four bit word. Hence the speed of operation of SIPO mode is same as that of SISO mode.

Block Diagram

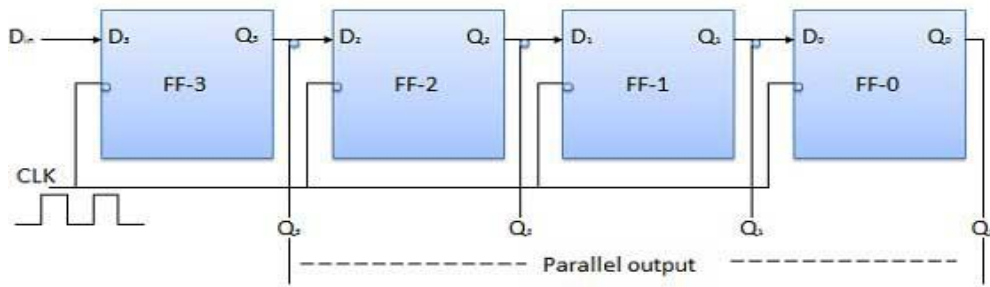

Parallel Input Serial Output (PISO)

- Data bits are entered in parallel fashion.
- The circuit shown below is a four bit parallel input serial output register.
- Output of previous Flip Flop is connected to the input of the next one via a combinational circuit.
- The binary input word B_0, B_1, B_2, B_3 is applied through the same combinational circuit.
- There are two modes in which this circuit can work namely - shift mode or load mode.


Load mode

When the shift/load bar line is low (0), the AND gate 2, 4 and 6 become active they will pass B_1, B_2, B_3 bits to the corresponding flip-flops. On the low going edge of clock, the binary input B_0, B_1, B_2, B_3 will get loaded into the corresponding flip-flops. Thus parallel loading takes place.

Shift mode

When the shift/load bar line is low (1), the AND gate 2, 4 and 6 become inactive. Hence the parallel loading of the data becomes impossible. But the AND gate 1,3 and 5 become active. Therefore the shifting of data from left to right bit by bit on application of clock pulses. Thus the parallel in serial out operation takes place.


Block Diagram

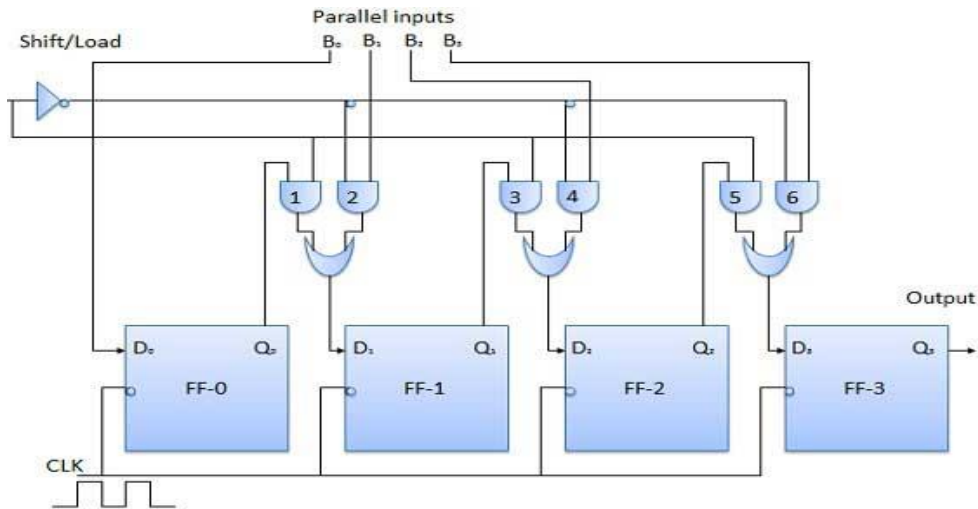

Parallel Input Parallel Output (PIPO)

In this mode, the 4 bit binary input B_0, B_1, B_2, B_3 is applied to the data inputs D_0, D_1, D_2, D_3 respectively of the four flip-flops. As soon as a negative clock edge is applied, the input binary bits will be loaded into the flip-flops simultaneously. The loaded bits will appear simultaneously to the output side. Only clock pulse is essential to load all the bits.


Block Diagram

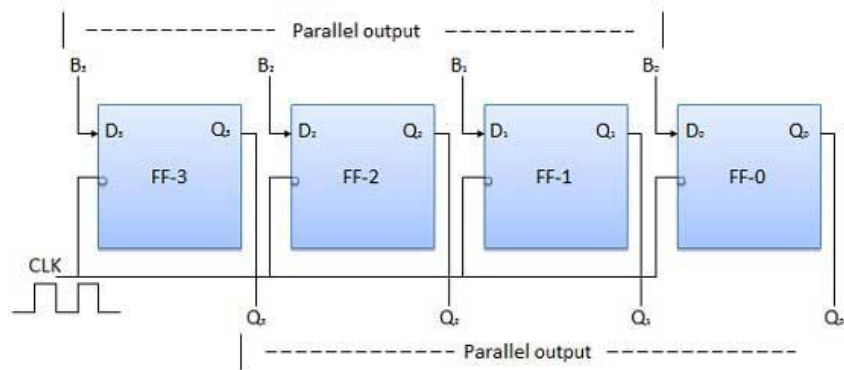

Bidirectional Shift Register

- If a binary number is shifted left by one position then it is equivalent to multiplying the original number by 2. Similarly if a binary number is shifted right by one position then it is equivalent to dividing the original number by 2.
- Hence if we want to use the shift register to multiply and divide the given binary number, then we should be able to move the data in either left or right direction.
- Such a register is called bi-directional register. A four bit bi-directional shift register is shown in fig.
- There are two serial inputs namely the serial right shift data input DR, and the serial left shift data input DL along with a mode select input (M).

Block Diagram

 

Operation

| S.N. | Condition | Operation |
|------|--|---|
| 1 | With $M = 1$ – Shift right operation | <p>If $M = 1$, then the AND gates 1, 3, 5 and 7 are enabled whereas the remaining AND gates 2, 4, 6 and 8 will be disabled.</p> <p>The data at D_R is shifted to right bit by bit from FF-3 to FF-0 on the application of clock pulses. Thus with $M = 1$ we get the serial right shift operation.</p> |
| 2 | With $M = 0$ – Shift left operation | <p>When the mode control M is connected to 0 then the AND gates 2, 4, 6 and 8 are enabled while 1, 3, 5 and 7 are disabled.</p> <p>The data at D_L is shifted left bit by bit from FF-0 to FF-3 on the application of clock pulses. Thus with $M = 0$ we get the serial right shift operation.</p> |

Universal Shift Register


A shift register which can shift the data in only one direction is called a uni-directional shift register. A shift register which can shift the data in both directions is called a bi-directional shift register. Applying the same logic, a shift register which can shift the data in both

directions as well as load it parallelly, is known as a universal shift register. The shift register is capable of performing the following operation –

- Parallel loading
- Left Shifting
- Right shifting

The mode control input is connected to logic 1 for parallel loading operation whereas it is connected to 0 for serial shifting. With mode control pin connected to ground, the universal shift register acts as a bi-directional register. For serial left operation, the input is applied to the serial input which goes to AND gate-1 shown in figure. Whereas for the shift right operation, the serial input is applied to D input.

Block Diagram

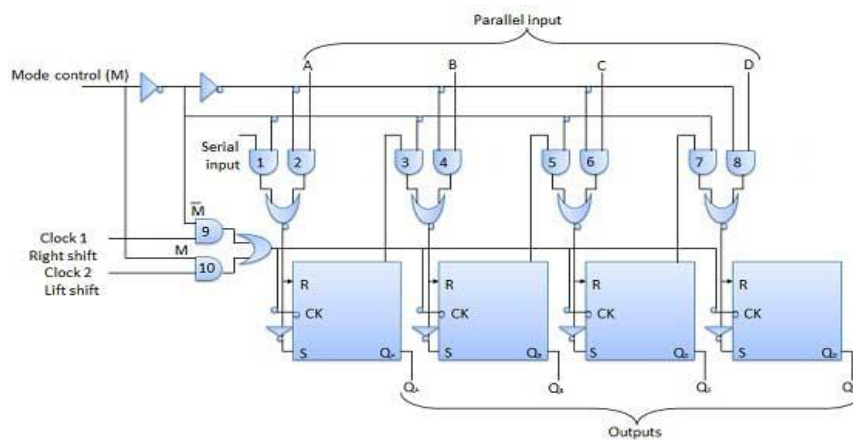

Counter


Counter is a sequential circuit. A digital circuit which is used for a counting pulses is known as counter. Counter is the widest application of flip-flops. It is a group of flip-flops with a clock signal applied. Counters are of two types.

- Asynchronous or ripple counters.
- Synchronous counters.

Asynchronous or ripple counters

The logic diagram of a 2-bit ripple up counter is shown in figure. The toggle (T) flip-flop are being used. But we can use the JK flip-flop also with J and K connected permanently to logic 1. External clock is applied to the clock input of flip-flop A and Q_A output is applied to the clock input of the next flip-flop i.e. FF-B.

Logical Diagram

 

Operation

| S.N. | Condition | Operation |
|------|---|---|
| 1 | Initially let both the FFs be in the reset state | $Q_B Q_A = 00$ initially |
| 2 | After 1st negative clock edge | <p>As soon as the first negative clock edge is applied, FF-A will toggle and Q_A will be equal to 1.</p> <p>Q_A is connected to clock input of FF-B. Since Q_A has changed from 0 to 1, it is treated as the positive clock edge by FF-B. There is no change in Q_B because FF-B is a negative edge triggered FF.</p> <p>$Q_B Q_A = 01$ after the first clock pulse.</p> |
| 3 | After 2nd negative clock edge | <p>On the arrival of second negative clock edge, FF-A toggles again and $Q_A = 0$.</p> <p>The change in Q_A acts as a negative clock edge for FF-B. So it will also toggle, and Q_B will be 1.</p> <p>$Q_B Q_A = 10$ after the second clock pulse.</p> |

| | | |
|---|--------------------------------------|--|
| 4 | After 3rd negative clock edge | <p>On the arrival of 3rd negative clock edge, FF-A toggles again and Q_A become 1 from 0.</p> <p>Since this is a positive going change, FF-B does not respond to it and remains inactive. So Q_B does not change and continues to be equal to 1.</p> <p>$Q_B Q_A = 11$ after the third clock pulse.</p> |
| 5 | After 4th negative clock edge | <p>On the arrival of 4th negative clock edge, FF-A toggles again and Q_A becomes 1 from 0.</p> <p>This negative change in Q_A acts as clock pulse for FF-B. Hence it toggles to change Q_B from 1 to 0.</p> <p>$Q_B Q_A = 00$ after the fourth clock pulse.</p> |

Truth Table

| Clock | Counter output | | State number | Deciimal Counter output |
|-----------|----------------|-------|--------------|-------------------------|
| | Q_B | Q_A | | |
| Initially | 0 | 0 | — | 0 |
| 1st | 0 | 1 | 1 | 1 |
| 2nd | 1 | 0 | 2 | 2 |
| 3rd | 1 | 1 | 3 | 3 |
| 4th | 0 | 0 | 4 | 0 |


Synchronous counters

If the "clock" pulses are applied to all the flip-flops in a counter simultaneously, then such a counter is called as synchronous counter.

2-bit Synchronous up counter

The J_A and K_A inputs of FF-A are tied to logic 1. So FF-A will work as a toggle flip-flop. The J_B and K_B inputs are connected to Q_A .

Logical Diagram

 

Operation

| S.N. | Condition | Operation |
|------|---|---|
| 1 | Initially let both the FFs be in the reset state | $Q_B Q_A = 00$ initially. |
| 2 | After 1st negative clock edge | <p>As soon as the first negative clock edge is applied, FF-A will toggle and Q_A will change from 0 to 1.</p> <p>But at the instant of application of negative clock edge, $Q_A, J_B = K_B = 0$. Hence FF-B will not change its state. So Q_B will remain 0.</p> <p>$Q_B Q_A = 01$ after the first clock pulse.</p> |
| 3 | After 2nd negative clock edge | <p>On the arrival of second negative clock edge, FF-A toggles again and Q_A changes from 1 to 0.</p> <p>But at this instant Q_A was 1. So $J_B = K_B = 1$ and FF-B will toggle. Hence Q_B changes from 0 to 1.</p> <p>$Q_B Q_A = 10$ after the second clock pulse.</p> |
| 4 | After 3rd negative clock edge | <p>On application of the third falling clock edge, FF-A will toggle from 0 to 1 but there is no change of state for FF-B.</p> |

| | | |
|---|--------------------------------------|--|
| | | $Q_B Q_A = 11$ after the third clock pulse. |
| 5 | After 4th negative clock edge | <p>On application of the next clock pulse, Q_A will change from 1 to 0 as Q_B will also change from 1 to 0.</p> <p>$Q_B Q_A = 00$ after the fourth clock pulse.</p> |

Classification of counters

Depending on the way in which the counting progresses, the synchronous or asynchronous counters are classified as follows –

- Up counters
- Down counters
- Up/Down counters

UP/DOWN Counter

Up counter and down counter is combined together to obtain an UP/DOWN counter. A mode control (M) input is also provided to select either up or down mode. A combinational circuit is required to be designed and used between each pair of flip-flop in order to achieve the up/down operation.

- Type of up/down counters
- UP/DOWN ripple counters
- UP/DOWN synchronous counter

UP/DOWN Ripple Counters

In the UP/DOWN ripple counter all the FFs operate in the toggle mode. So either T flip-flops or JK flip-flops are to be used. The LSB flip-flop receives clock directly. But the clock to every other FF is obtained from ($Q = \bar{Q}$) output of the previous FF.


- **UP counting mode (M=0)** – The Q output of the preceding FF is connected to the clock of the next stage if up counting is to be achieved. For this mode, the mode select input M is at logic 0 (M=0).
- **DOWN counting mode (M=1)** – If M = 1, then the Q bar output of the preceding FF is connected to the next FF. This will operate the counter in the counting mode.

Example

3-bit binary up/down ripple counter.

- 3-bit – hence three FFs are required.
- UP/DOWN – So a mode control input is essential.
- For a ripple up counter, the Q output of preceding FF is connected to the clock input of the next one.
- For a ripple up counter, the Q output of preceding FF is connected to the clock input of the next one.
- For a ripple down counter, the Q bar output of preceding FF is connected to the clock input of the next one.
- Let the selection of Q and Q bar output of the preceding FF be controlled by the mode control input M such that, If M = 0, UP counting. So connect Q to CLK. If M = 1, DOWN counting. So connect Q bar to CLK.

Block Diagram

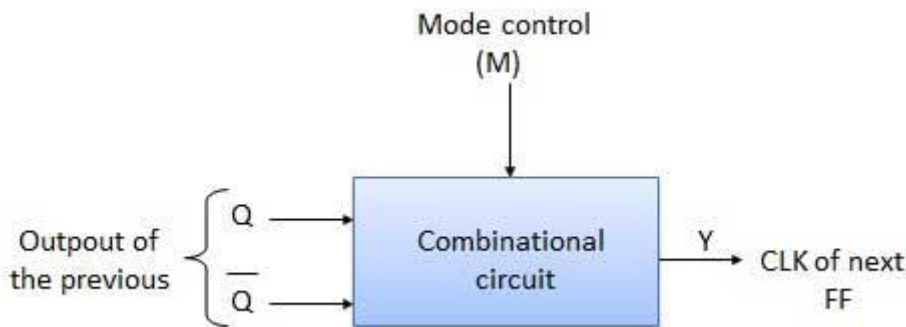

Truth Table

| Inputs | | | Outputs |
|--------|---|----------------|---------|
| M | Q | \overline{Q} | Y |
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

Y = Q for up counter
 Y = \overline{Q} for up counter

Operation

| S.N. | Condition | Operation |
|------|--|---|
| 1 | Case 1 – With M = 0 (Up counting mode) | <p>If $M = 0$ and $\bar{M} = 1$, then the AND gates 1 and 3 in fig. will be enabled whereas the AND gates 2 and 4 will be disabled.</p> <p>Hence Q_A gets connected to the clock input of FF-B and Q_B gets connected to the clock input of FF-C.</p> <p>These connections are same as those for the normal up counter. Thus with $M = 0$ the circuit work as an up counter.</p> |
| 2 | Case 2: With M = 1 (Down counting mode) | <p>If $M = 1$, then AND gates 2 and 4 in fig. are enabled whereas the AND gates 1 and 3 are disabled.</p> <p>Hence \bar{Q}_A gets connected to the clock input of FF-B and \bar{Q}_B gets connected to the clock input of FF-C.</p> <p>These connections will produce a down counter. Thus with $M = 1$ the circuit works as a down counter.</p> |

Modulus Counter (MOD-N Counter)

The 2-bit ripple counter is called as MOD-4 counter and 3-bit ripple counter is called as MOD-8 counter. So in general, an n-bit ripple counter is called as modulo-N counter. Where, MOD number = 2^n .

Type of modulus

- 2-bit up or down (MOD-4)
- 3-bit up or down (MOD-8)
- 4-bit up or down (MOD-16)

Application of counters


- Frequency counters
- Digital clock
- Time measurement

- A to D converter
- Frequency divider circuits
- Digital triangular wave generator.

State Reduction & Assignment

Sometimes certain properties of sequential circuits may be used to reduce the number of gates and flip-flops during the design. The problem of state reduction is to find ways of reducing the number of states in a sequential circuit, while keeping the external input-output relationships unchanged.

 For example, suppose a sequential circuit is specified by the following seven-state diagram:



There are an infinite number of input sequences that may be applied; each results in a unique output sequence. Consider the input sequence 01010110100 starting from the initial state a:

| | | | | | | | | | | | | |
|--------|---|---|---|---|---|---|---|---|---|---|---|---|
| state | a | a | b | c | d | e | f | f | g | f | g | a |
| input | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | |
| output | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | |

An algorithm for the state reduction quotes that:

“Two states are said to be equivalent if, for each member of the set of inputs, they give exactly the same output and send the circuit either to the same state or to an equivalent state.”

Now apply this algorithm to the state table of the circuit:

| Present State | Next State | | Output | |
|---------------|------------|----------|---------|---------|
| | $x = 0$ | $x = 1$ | $x = 0$ | $x = 1$ |
| <i>a</i> | <i>a</i> | <i>b</i> | 0 | 0 |
| <i>b</i> | <i>c</i> | <i>d</i> | 0 | 0 |
| <i>c</i> | <i>a</i> | <i>d</i> | 0 | 0 |
| <i>d</i> | <i>e</i> | <i>f</i> | 0 | 1 |
| <i>e</i> | <i>a</i> | <i>f</i> | 0 | 1 |
| <i>f</i> | <i>g</i> | <i>f</i> | 0 | 1 |
| <i>g</i> | <i>a</i> | <i>f</i> | 0 | 1 |

States *g* and *e* both go to states *a* and *f* and have outputs of 0 and 1 for $x = 0$ and $x = 1$, respectively.

The procedure for removing a state and replacing it by its equivalent is demonstrated in the following table:


| Present State | Next State | | Output | |
|---------------|------------|----------|---------|---------|
| | $x = 0$ | $x = 1$ | $x = 0$ | $x = 1$ |
| <i>a</i> | <i>a</i> | <i>b</i> | 0 | 0 |
| <i>b</i> | <i>c</i> | <i>d</i> | 0 | 0 |
| <i>c</i> | <i>a</i> | <i>d</i> | 0 | 0 |
| <i>d</i> | <i>e</i> | <i>f</i> | 0 | 1 |
| <i>e</i> | <i>a</i> | <i>f</i> | 0 | 1 |
| <i>f</i> | <i>e</i> | <i>f</i> | 0 | 1 |

Thus, the row with present state *g* is removed and stage *g* is replaced by state *e* each time it occurs in the next state columns. Present state *f* now has next states *e* and *f* and outputs 0 and 1 for $x = 0$ and $x = 1$. The same next states and outputs appear in the row with present state *d*. Therefore, states *f* and *d* are equivalent and can be removed and replaced with *d*.

The final reduced state table is:

| Present State | Next State | | Output | |
|---------------|------------|----------|---------|---------|
| | $x = 0$ | $x = 1$ | $x = 0$ | $x = 1$ |
| <i>a</i> | <i>a</i> | <i>b</i> | 0 | 0 |
| <i>b</i> | <i>c</i> | <i>d</i> | 0 | 0 |
| <i>c</i> | <i>a</i> | <i>d</i> | 0 | 0 |
| <i>d</i> | <i>e</i> | <i>d</i> | 0 | 1 |
| <i>e</i> | <i>a</i> | <i>d</i> | 0 | 1 |

 The state diagram for the above reduced table is:



This state diagram satisfies the original input output specifications.

Applying the input sequence previously used, the following list is obtained:


| | | | | | | | | | | | | |
|--------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|
| state | <i>a</i> | <i>a</i> | <i>b</i> | <i>c</i> | <i>d</i> | <i>e</i> | <i>d</i> | <i>d</i> | <i>e</i> | <i>d</i> | <i>e</i> | <i>a</i> |
| input | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | |
| output | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | |

Note that the same output sequence results, although the state sequence is different.

Analysis Procedure of Asynchronous Sequential Circuits

- Do not use pulses. The change of internal state occurs when there is a change in the input variable.
- Their memory elements are either unclocked flip flops or time delay elements.
- They often resemble combinational circuit with feedback.
- Their synthesis is much difficult than the synthesis of clocked synchronous sequential circuit.
- They are used when speed of operation is important.

 The communication of two units, with each unit having its own independent clock, must be done with asynchronous circuits.



There are n input variables, m output variables, and k internal states.

The present state variables (y_1 and y_2) are called secondary variables. The next state variables (Y_1 and Y_2) are called excitation variables.


Fundamental mode operation assumes that the input signals change one at a time and only when the circuit is in a condition.

1. Analysis Procedure

The analysis of asynchronous sequential circuits proceeds in much the same way as that of clocked synchronous sequential circuits. From a logic diagram, Boolean expressions are written and then transferred into tabular form.

 1. Transition Table

An example of an asynchronous sequential circuit is shown below:



The analysis of the circuit starts by considering the excitation variables (y_1 and y_2).


As outputs and the secondary variables (y_1 and y_2) as inputs.

The Boolean expressions are:


$$Y_1 = xy_1 + x'y_2$$

$$Y_2 = xy'_1 + x'y_2$$

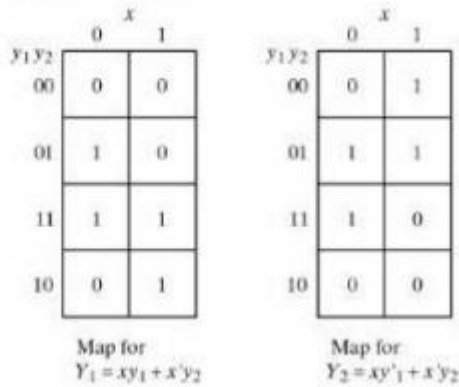The next step is to plot the Y_1 and Y_2 functions in a map:



 Combining the binary values in corresponding squares the following transition table is obtained.



The transition table shows the values of $Y=Y_1Y_2$ inside each square. Those where $Y=y$ are circled to indicate a stable condition.

The circuit has four stable total states $-y_1y_2x = 000, 011, 110,$ and 100 and four unstable total states $001, 010, 111,$ and 100 .


The state table of the circuit shown below:

| Present State | Next State | | | |
|---------------|------------|---|---------|---|
| | $x = 0$ | | $x = 1$ | |
| 0 0 | 0 | 0 | 0 | 1 |
| 0 1 | 1 | 1 | 0 | 1 |
| 1 0 | 0 | 0 | 1 | 0 |
| 1 1 | 1 | 1 | 1 | 0 |

The table provides the same information as the transition table.

 
2. Flow Table

In a flow states are named by letter symbols. Examples of flow tables are as follows.




In order to obtain the circuit described by a flow table, it is necessary to assign to each state distinct value.

 This assignment converts the flow table into a transition table. This is shown below:



 
The resulting logic diagram is shown below:



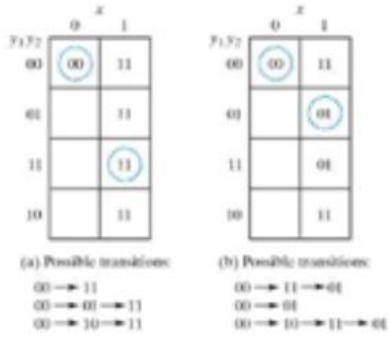3. Race Conditions


A race condition exists in an asynchronous circuit when two or more binary state variables change value in response to a change in an input variable, when unequal delays are encountered a race condition may cause the state variable to change in an unpredictable manner.

If the final stable state that the circuit reaches does not depend on the order in which the state variable change, the races are illustrated in the transition tables below:



7

 The transition tables below illustrate critical races:



Races can be avoided by directing the circuit through a unique sequence of intermediate unstable states when a circuit does that, it is said to have a cycle. Examples of cycles are:

